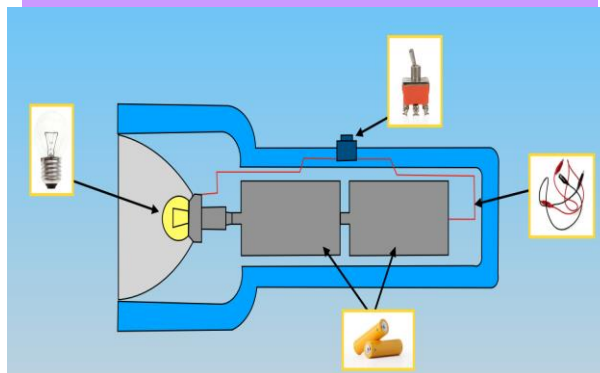


DT: Torches




General Knowledge

The battery and the bulb are both essential components in a circuit for a torch. Without the battery, there would be no power, and without the bulb, there would be no light. For a bulb to shine, the energy from the battery has to be able to flow around the circuit in a continuous, unbroken loop, so the switch needs to be closed. This is called a complete circuit.



Be the BEST you can be

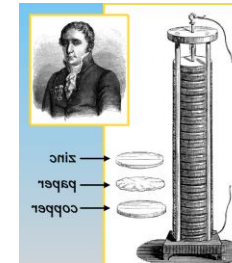

Which do you think was invented first - the battery or the bulb?

Making secure connections



Handmade switches



Commercial switches

